

# 电子电路手册

## Electronic Circuits Manual

丁毅

(中国科学院大学, 北京 100049)

Yi Ding

*(University of Chinese Academy of Sciences, Beijing 100049, China)*

2024.11 – ...

# 序言

# Preface

# Contents

序言	I
Preface	II
Contents	III
1 Capacitance	1
1.1 Capacitance Multiplier . . . . .	1
1.2 Capacitance Measurement . . . . .	1
1.3 Variable Capacitance . . . . .	1
Reference	1

# Chapter 1 Capacitance

## 1.1 Capacitance Multiplier

This part refers to references [?] and [?]. Below are two basic concepts for capacitance multiplication:

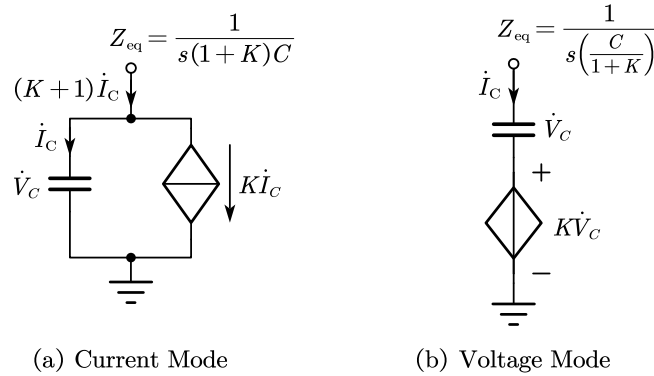


Figure 1.1: Basic Capacitance Multiplier Circuits

Thus, we obtain the equivalent capacitance as:

$$\text{Current Mode: } C_{eq} = (1 + K)C \Rightarrow \begin{cases} C_{eq} > C, & K > 0 \\ C_{eq} < C, & K < 0 \end{cases} \quad (1.1)$$

$$\text{Voltage Mode: } C_{eq} = \frac{C}{1 + K} \Rightarrow \begin{cases} C_{eq} < C, & K > 0 \\ C_{eq} > C, & K < 0 \end{cases} \quad (1.2)$$

A simple implementation of cap multiplier, depicted in Fig.1.2, combining a unit-gain buffer (voltage follower) and an inverting amplifier, is a voltage mode circuit. yielding the equivalent capacitance:

$$C_{eq} = \frac{C}{1 + K} = \frac{1}{1 - \frac{R_2}{R_1}} = \frac{R_1}{R_1 - R_2} C \quad (1.3)$$

where  $K = -\frac{R_2}{R_1}$  is the closed-loop gain of the inverting amplifier. Since inverting amplifier has a low input impedance, the unit-gain buffer is a necessary. To change it into a two-terminal element, just replace GND with the negative terminal of the input voltage, e.g.  $V_{in,-}$ .

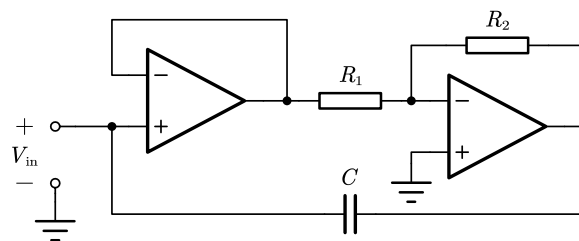


Figure 1.2: A Simple Implementation of Capacitance Multiplier

## 1.2 Capacitance Measurement

## 1.3 Variable Capacitance