

## Laboratory 2: 2024.11.21 - 2024.12.12

### 14.1 Pre-Lab

#### (1) Voltage-Voltage Characteristics of Inverting Amplifier

The output voltage  $V_{\text{out}}$  as a function of input voltage  $V_{\text{in}}$  is shown in Fig. 14.1, where  $V_T$  is the threshold voltage of the MOSFET.

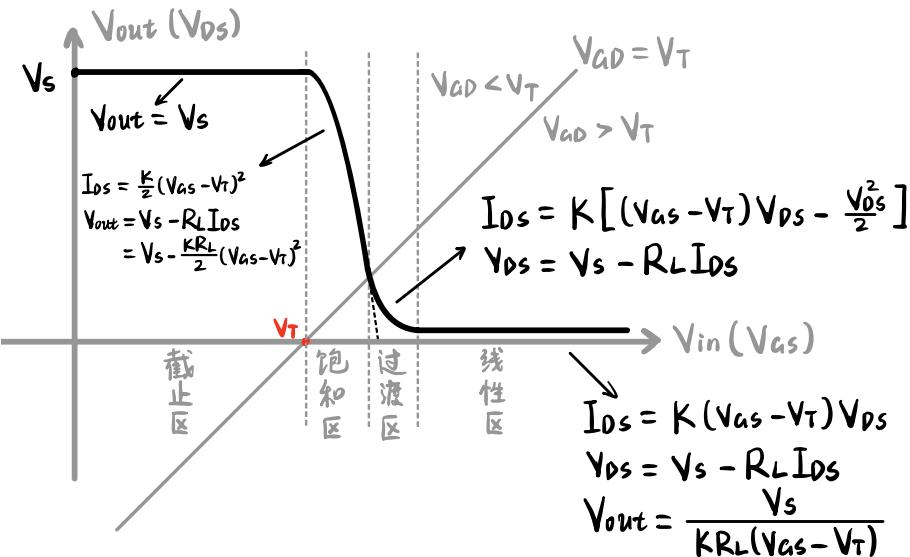


Figure 14.1: Voltage-Voltage Characteristics of Inverting Amplifier

For easy reference, we summarize the formula as:

$$V_{\text{out}} = \begin{cases} V_s, & V_{\text{GS}} \in [0, V_T] \\ V_s - \frac{KR_L}{2}(V_{\text{GS}} - V_T)^2, & V_{\text{GS}} \in [V_T, V_0] \\ V_{\text{GS}} - V_T + \frac{1-\sigma}{KR_L}, & V_{\text{GS}} \in [V_0, V_0 + \Delta V] \\ \frac{V_s}{KR_L(V_{\text{GS}} - V_T)}, & V_{\text{GS}} \in [V_0 + \Delta V, V_{\text{max}}] \end{cases} \quad (14.1)$$

Where  $V_0$  is the second solution  $V_{\text{GS},2}$  of equations:

$$\begin{cases} V_{\text{GS}} = V_s - \frac{KR_L}{2}(V_{\text{GS}} - V_T)^2 \\ V_{\text{GD}} = V_T \end{cases} \implies V_0 = \frac{\sqrt{2KR_LV_s + 1} + KR_LV_T - 1}{KR_L} \quad (14.2)$$

And  $\sigma$  is the discriminant of the quadratic equation:

$$\sigma = \sqrt{K^2R_L^2V_{\text{GS}}^2 + 2KR_L(1 - KR_LV_T)V_{\text{GS}} + [K^2R_L^2V_T^2 - 2KR_L(V_T + V_s) + 1]} \quad (14.3)$$

When the input voltage  $V_{\text{in}}(V_{\text{GS}}) > V_0$  is large enough, i.e.  $V_{\text{in}} \geq V_0 + \Delta V$ , an approximation can be made:

$$I_{\text{DS}} \approx K(V_{\text{GS}} - V_T)V_{\text{ds}} \implies V_{\text{out}} = \frac{V_s}{KR_L(V_{\text{GS}} - V_T)} \quad (14.4)$$

## (2) Small Voltage Gain of Inverting Amplifier

We have already driven the small signal voltage gain during the last homework. Assuming the small AC input voltage is  $u_{\text{in}}$ , and MOS is biased into saturation region, it follows that:

$$A = \frac{u_{\text{out}}}{u_{\text{in}}} = -g_m R_L = -K(V_{\text{GS}} - V_{\text{T}}) R_L \quad (14.5)$$

## (3) RC Transient Process

By the three-element method, we can obtain:

$$V_{\text{out}} = \frac{R_2 V_{\text{I}}}{R_1 + R_2} \left(1 - e^{-\frac{t}{\tau}}\right), \quad \tau = (R_1 \parallel R_2) C = \frac{R_1 R_2}{R_1 + R_2} C \quad (14.6)$$

## (4) Transient Time

Given  $V_{\text{T}}$  in the range  $[0, V_{\text{S}}]$  ( $V_{\text{S}} = \frac{R_2 V_{\text{I}}}{R_1 + R_2}$ ), the time where  $V_{\text{out}}$  reaches  $V_{\text{T}}$  is:

$$\Delta t = \tau \ln \left( \frac{V_{\text{S}}}{V_{\text{S}} - V_{\text{T}}} \right), \quad \tau = \frac{R_1 R_2}{R_1 + R_2} C, \quad V_{\text{S}} = \frac{R_2 V_{\text{I}}}{R_1 + R_2} \quad (14.7)$$

## 14.2 In-Lab

### (1) Static Input-Output Relationship of Inverting Amplifier

#### Measure In-Out Voltage Relationship

Construct the circuit in Fig.14.2, then we can obtain the voltage relationship shown in Fig.14.3.

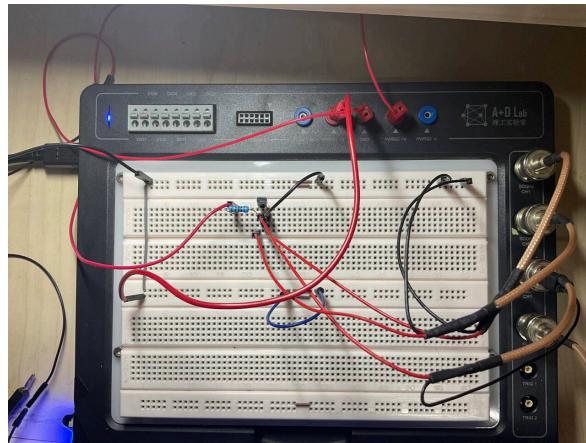


Figure 14.2: Measure In-Out Voltage Relationship

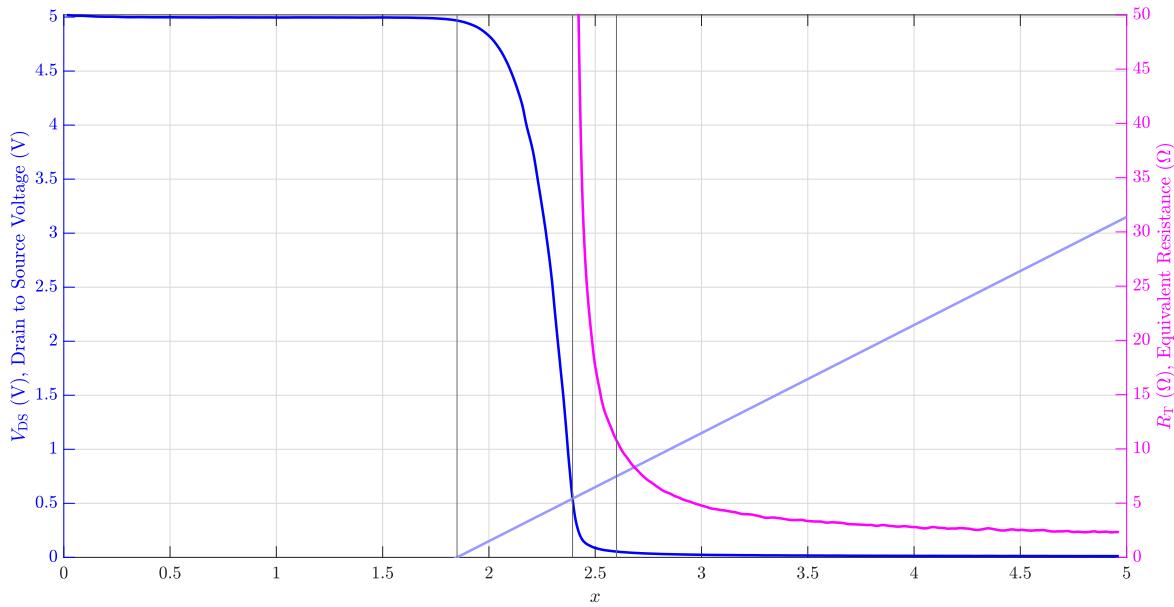


Figure 14.3: Operational Characteristics of Inverting Amplifier

### The Threshold of The MOSFET

With  $V_S = 5.0185$  V,  $R_L = 1$  KΩ (998 Ω) and the data obtained in the last section, we can get the threshold voltage of the MOSFET:

$$V_T = 1.85 \text{ V}, \quad V_0 = 2.3934 \text{ V}, \quad \Delta V = 0.2066 \text{ V} \quad (14.8)$$

### Tables of Input-Output Voltage


Table 14.1: Input-Output Voltage Relationship

Output (V)	5	4	3	2	1	0.0116
Input (V)	0.2765	2.1767	2.2686	2.3238	2.3712	4.9599

### (2) Small Signal Voltage Gain

#### Voltage Gain of Inverting Amplifier

With the data measured in section (1), we can derived the voltage gain  $A_v = \frac{dV_{DS}}{dV_{GS}}$  via matrix difference (see Fig.14.4).

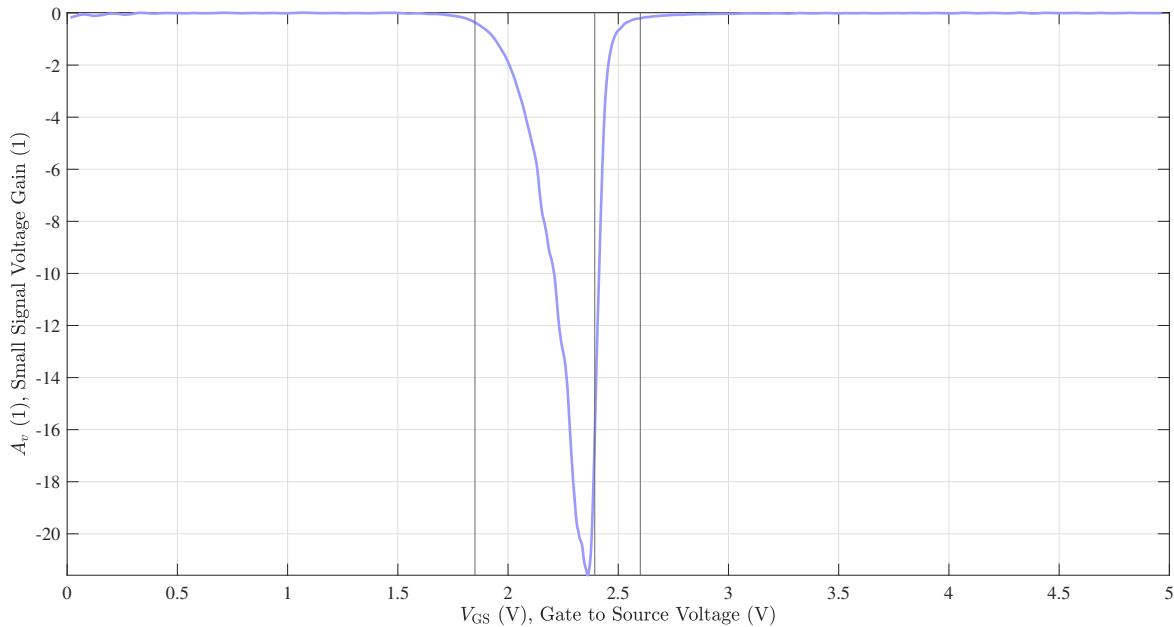

**Figure 14.4: Small Signal Voltage Gain of Inverting Amplifier**

Since transconductance satisfies  $A = -g_m R_L$ , we can also get the transconductance by dividing the limiting resistance  $R_L = 1 \text{ K}\Omega$  ( $998 \Omega$ ).

Construct the circuit to measure the voltage gain where the output voltage is 2 V and the sine wave has 50 mV amplitude (from -50 mV to +50 mV). The measured result and the data in Fig.14.4 is:

$$(A_v)_{\text{meas}} = \frac{-1.0056 \text{ V}}{50 \text{ mV}} = -20.1120, \quad (A_v)_{\text{fig}} = -20.1513 \quad (14.9)$$

As we can see, almost no deviation.

### Clipping Distortion

Set the amplitude of sine wave to 50 mV ( $[-50 \text{ mV}, +50 \text{ mV}]$ ), the lower and upper bias limits are (see Fig.14.5 and Fig.14.6):

$$V_{\text{bias,min}} = 2.00 \text{ V}, \quad V_{\text{bias,max}} = 2.39 \text{ V} \quad (14.10)$$



Figure 14.5: The Lower Limit of The Input Bias Voltage

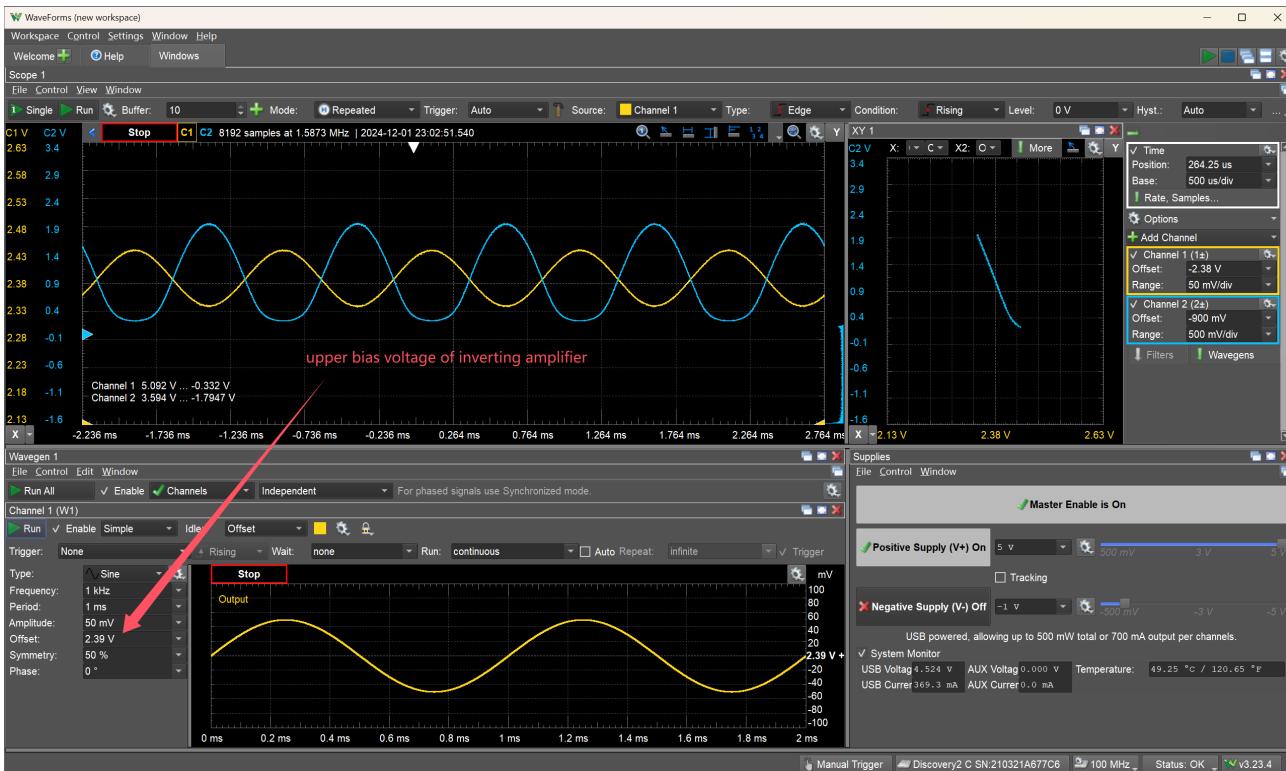


Figure 14.6: The Upper Limit of The Input Bias Voltage

### (3) The Delay of Inverting Amplifier as a Digital Inverter

#### Measure The Gate to Source Capacitance of Inverting Amplifier

Use a  $500\text{ K}\Omega$  resistor and a  $30\text{ K}\Omega$  resistor to measure the gate to source capacitance  $C_{GS}$  of the MOSFET, respectively. The measured results are:

$$R_L = 500\text{ K}\Omega, \lim_{t \rightarrow 0^+} \frac{dV_{out}}{dt} = 57070.3 \text{ V} \cdot \text{s}^{-1}, V_{steady} = 3.3198 \text{ V} \implies C = \frac{V_0}{R_L k_0^+} = 116.3407 \mu\text{F} \quad (14.11)$$

$$R_L = 30.0\text{ K}\Omega, \lim_{t \rightarrow 0^+} \frac{dV_{out}}{dt} = 948889.8 \text{ V} \cdot \text{s}^{-1}, V_{steady} = 4.9032 \text{ V} \implies C = \frac{V_0}{R_L k_0^+} = 172.2434 \mu\text{F} \quad (14.12)$$



Figure 14.7: Gate to Source Capacitance of 2N7000,  $R_L = 500\text{ K}\Omega$


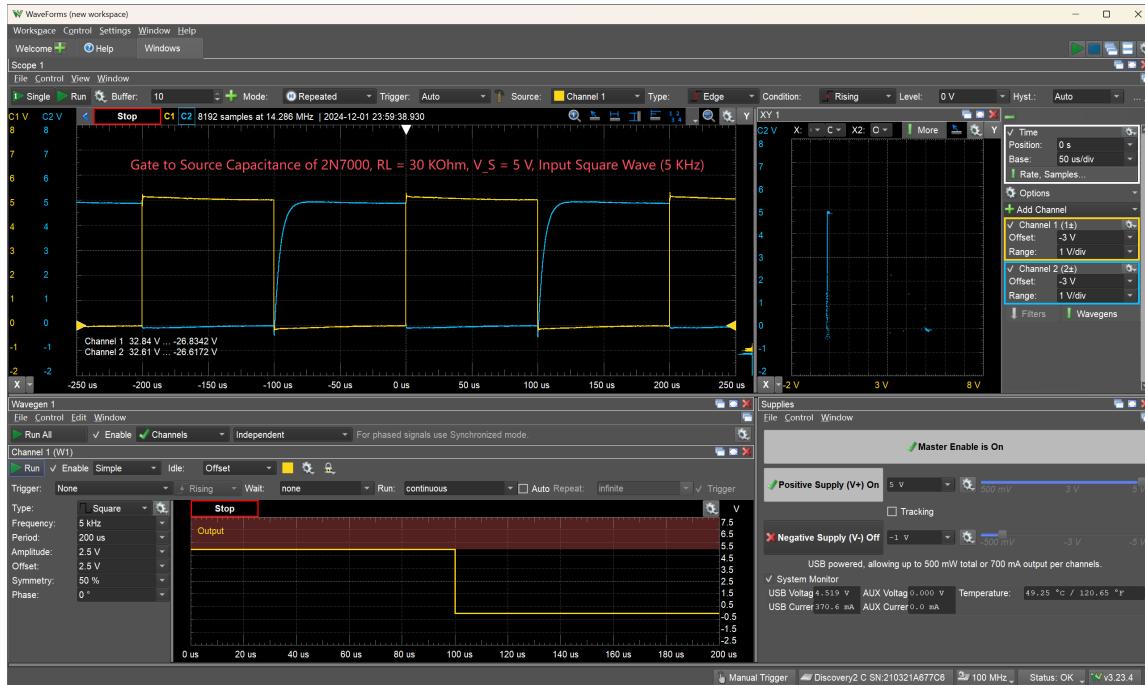


Figure 14.8: Gate to Source Capacitance of 2N7000,  $R_L = 30 \text{ k}\Omega$

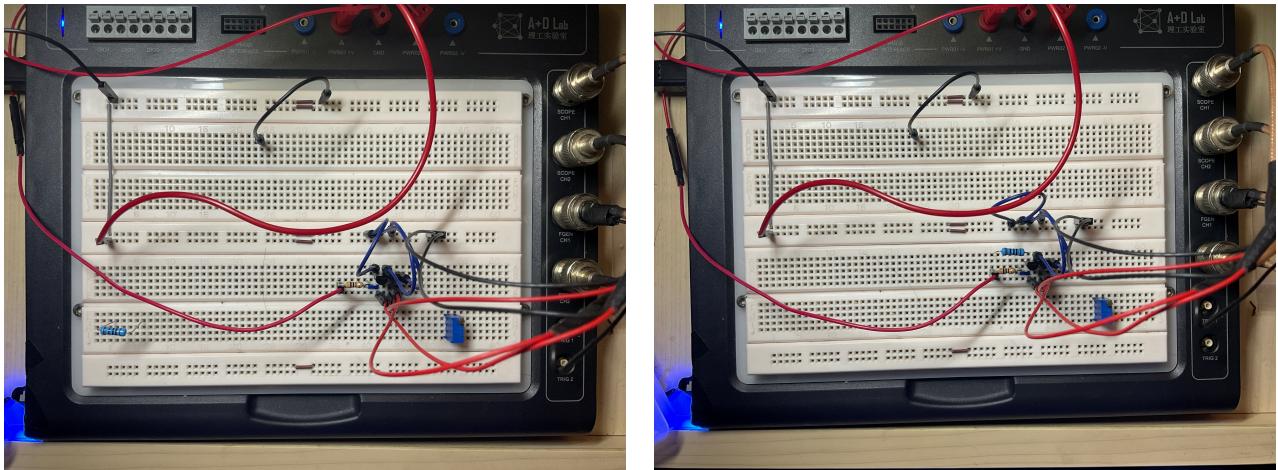It is puzzling that  $C = 100 \text{ pF}$  with  $R_L = 500 \text{ k}\Omega$ . Actually, with the resistance  $R_L = 500 \text{ k}\Omega$ , the steady voltage  $V_0$  is limited to 3.3198 V (see Fig.14.7), which is not the expected value. Why is it like that? Because the oscilloscope input resistance is not large enough. We keep this to the Post-Lab,



(a) The Gate to Source Capacitance of Inverting Amplifier

(b) The Delay of Inverting Amplifier as a Digital Inverter

Figure 14.9: In-Lab 3.1 and In-Lab 3.2

### Measure The Delay of Inverting Amplifier

With  $R_{L,1} = 30 \text{ k}\Omega$  and  $R_{L,2} = 1 \text{k}\Omega$ , construct the circuit in Fig.14.9 (b), obtain the delay time of the inverting amplifier as a digital inverter (see Fig.14.10 and Fig.14.11).

$$\text{start to fall: } \Delta t_1 = 1.504 \mu\text{s}, \quad \text{reach low: } \Delta t_2 = 3.799 \mu\text{s} \quad (14.13)$$

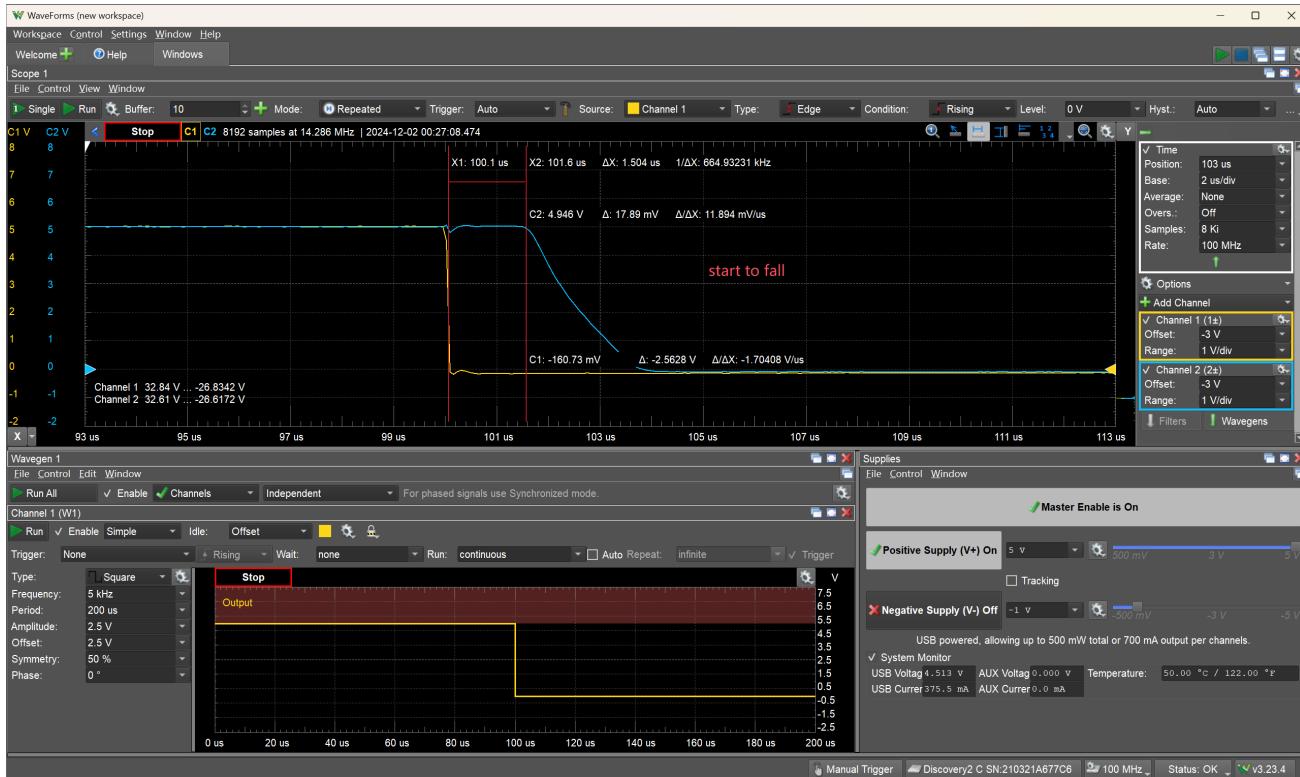


Figure 14.10: The Output Voltage Starts to Fall

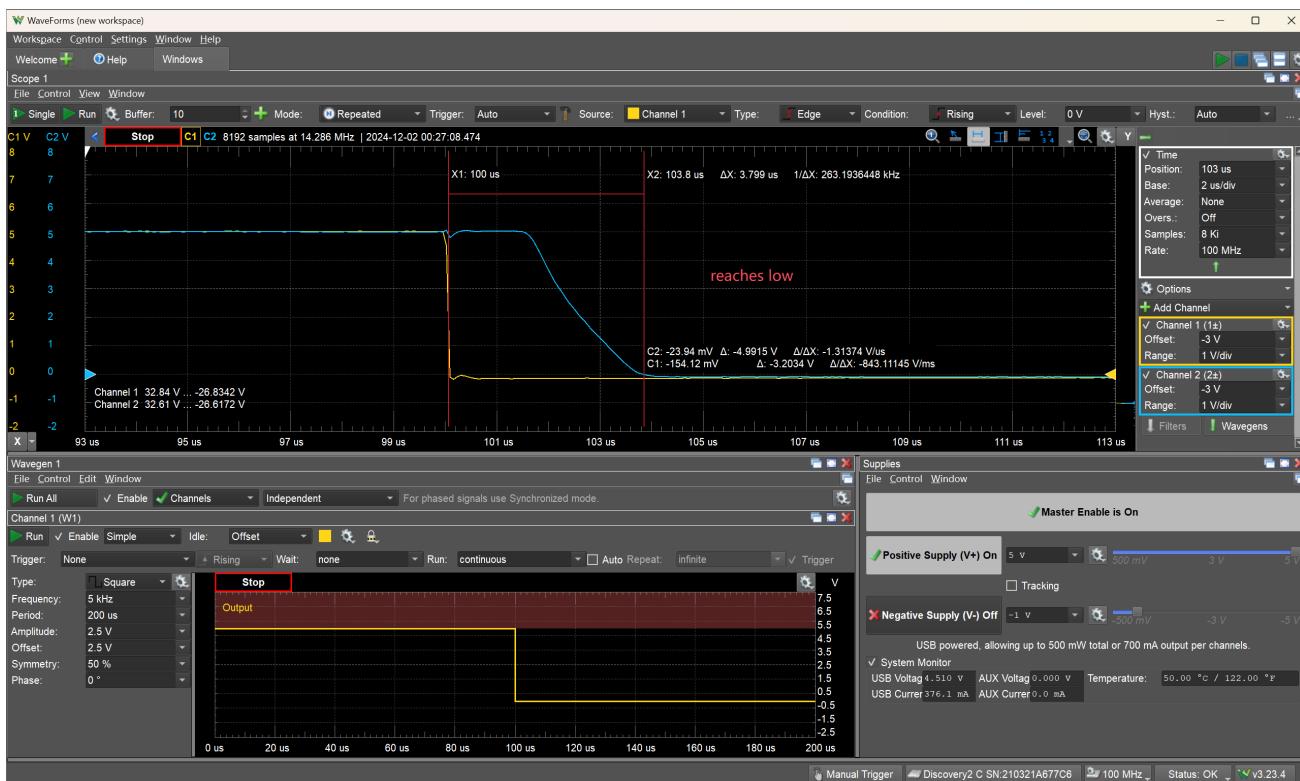


Figure 14.11: The Output Voltage Reaches to Low

It is interesting that resonance phenomena occurs, see Fig.14.12 and Fig.14.13.

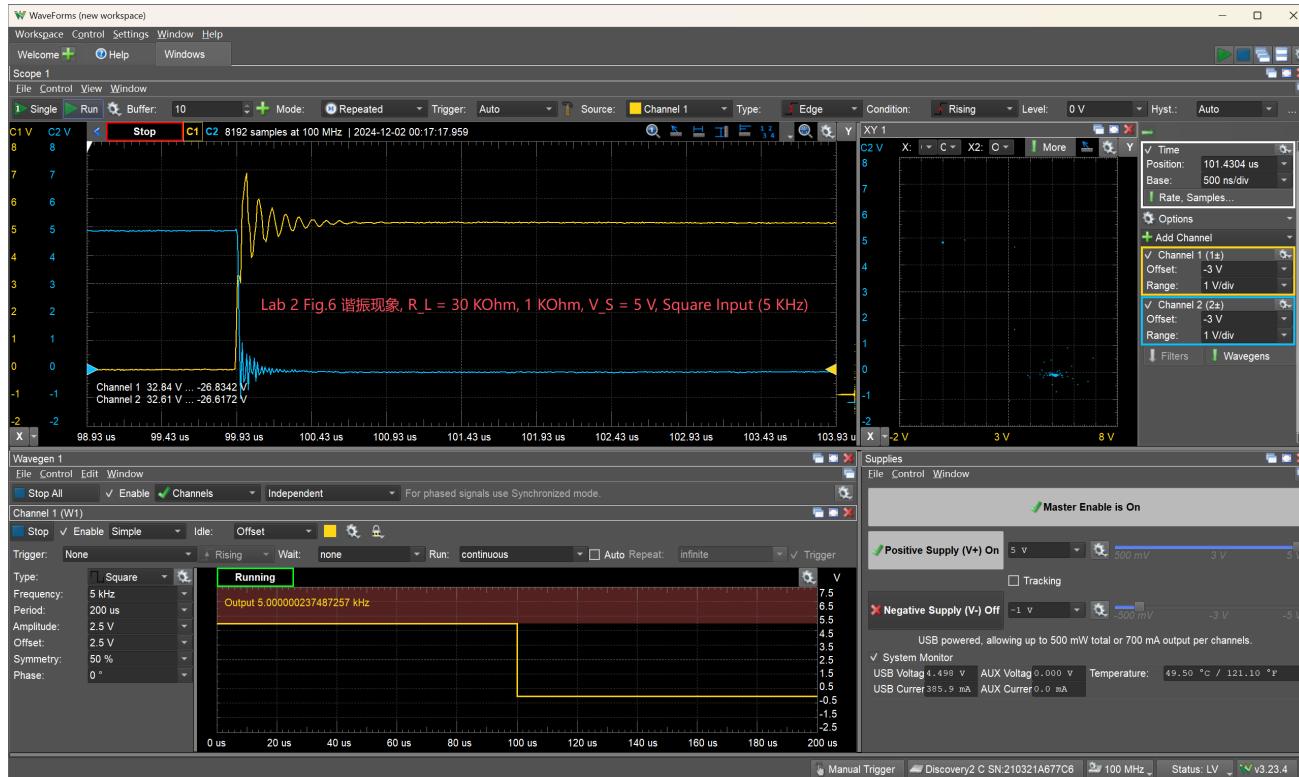


Figure 14.12: Input Voltage (Yellow) and Output Voltage (Blue) of The First MOS

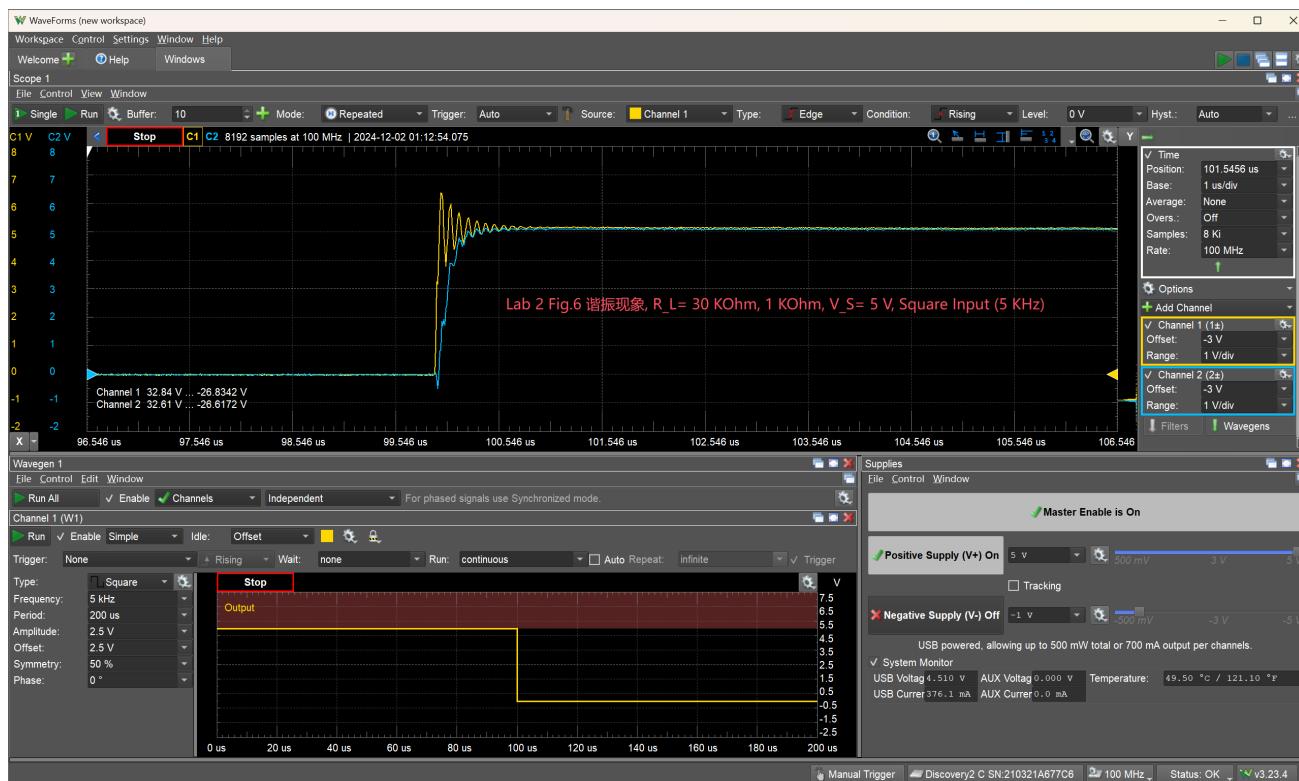


Figure 14.13: Input Voltage (Yellow) and Output Voltage (Blue) of The Second MOS

## 14.3 Post-Lab


### (1) Voltage-Voltage Characteristics Comparison

#### Transconductance Sensitivity $K$


Use the voltage-voltage characteristics data in section (1) to calculate the transconductance sensitivity  $K$  of the MOSFET:

$$\begin{cases} I_{DS} = \frac{K}{2} (V_{GS} - V_T)^2 \\ V_{DS} = V_S - I_{DS} R_L \end{cases} \implies K = \frac{2(V_S - V_{DS})}{R_L (V_{GS} - V_T)^2} \quad (14.14)$$

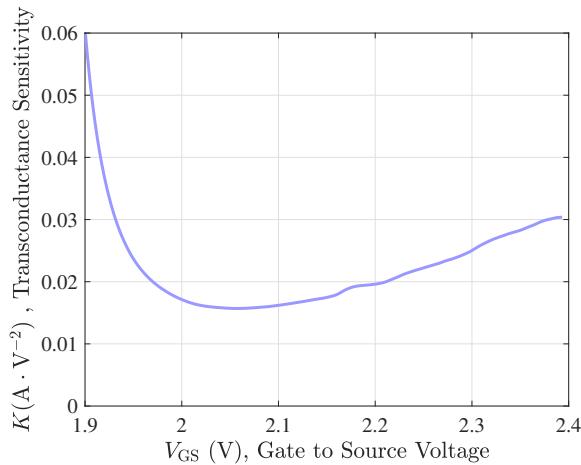Where  $V_T = 1.85$  V,  $R_L = 1$  KΩ (998 Ω) and  $V_S = 5.0185$  V. Plot the curve  $K = K(V_{GS})$ , as shown in Fig.14.14 (a):



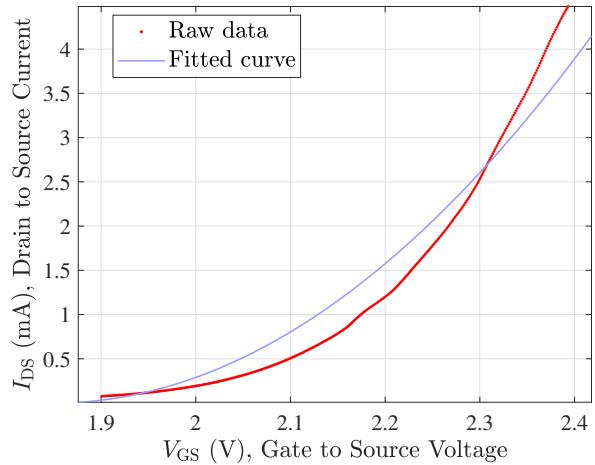(a) Transconductance Sensitivity  $K$  as a Function of  $V_{GS}$



(b) Drain to Source Current as a Function of  $V_{GS}$

Figure 14.14: Transconductance Sensitivity

As we can see,  $K$  is not a ideal constant value. So we try fitting  $I_{DS}$  as a function of  $V_{DS}$ , and the result is shown in Fig.14.14 (b),  $R^2 = 0.9511$ .

$$I_{DS} = \frac{K}{2} (V_{GS} - V_T)^2, \quad K = 0.02572 \text{ A} \cdot \text{V}^{-2}, \quad V_T = 1.85 \text{ V} \quad (14.15)$$

It is funny that the fitting result is excellent if we use  $I_{DS} = \frac{K}{2} (V_{GS} - V_T)^3$ , which has a high  $R^2 = 0.9977$ .

#### Comparison of Operational Characteristics

With the four parameters  $V_T = 1.85$  V,  $K = 0.02572 \text{ A} \cdot \text{V}^{-2}$ ,  $V_S = 5$  V and  $R_L = 1$  KΩ (998 Ω), we can compute and plot the theoretical operational characteristics of the inverting amplifier, as shown in Fig.14.15. Below are the other parameters for our theoretical model:

$$V_0 = \frac{\sqrt{2KR_LV_S + 1} + KR_LV_T - 1}{KR_L} = 2.4376 \text{ V}, \quad \Delta V = 1.5(V_0 - V_T) = 0.8814 \text{ V} \quad (14.16)$$

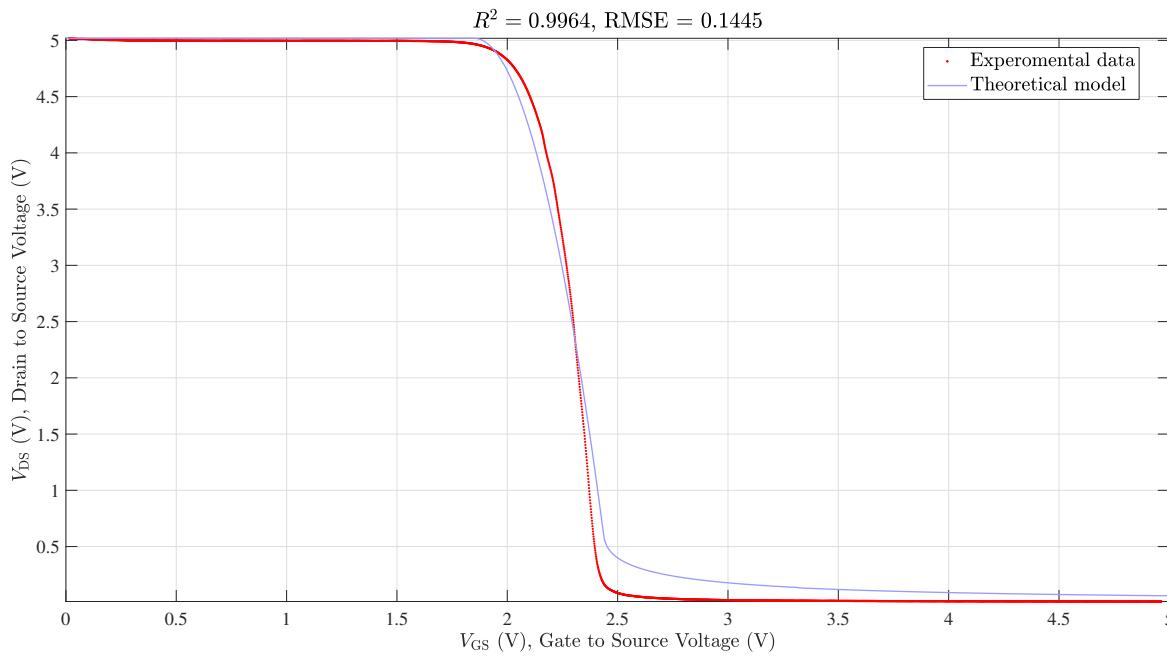


Figure 14.15: Operational Characteristics Comparison

## (2) Small Signal Voltage Gain

The voltage gain  $A_v$  measured during In-Lab 2-2 (section (2)), by the operational characteristics obtained in In-Lab 2-1 (section (1)) and the theoretical module from Pre-Lab are respectively (at Output  $V_{GS} = 2$  V):

Table 14.2: Voltage Gain at Output 2 V by Different Methods

By Experimental Measurement	By Operational Characteristics	By Theoretical Op Characteristics
-20.1120	-20.1513	-12.1670

## (3) Capacitance and Delay Analysis

### Total Input Capacitance

In Fig.14.7, we have seen that the output voltage drops to 3.3198 V, when  $R_L = 500 \text{ k}\Omega$  and  $V_S = 5 \text{ V}$ . It follows that:

$$V_{\text{out}} = \frac{R_{\text{osci}}}{R_{\text{osci}} + R_L} V_S \implies R_{\text{osci}} = \frac{R_L}{\frac{V_S}{V_{\text{out}}} - 1} = 987.9 \text{ k}\Omega \approx 1 \text{ M}\Omega \quad (14.17)$$

Assuming  $V_{\text{source}} = 5 \text{ V}$ , we can obtain the total input capacitance, including GS capacitance  $C_{\text{GS}}$  and oscilloscope input capacitance  $C_{\text{osci}}$ :

$$\begin{cases} k_{0+} = \frac{V_{\text{steady}}}{\tau} \\ V_{\text{steady}} = \frac{R_{\text{osci}}}{R_{\text{osci}} + R_L} \cdot V_{\text{source}} \\ \tau = (R_{\text{osci}} \parallel R_L)(C_{\text{GS}} + C_{\text{osci}}) \end{cases} \implies C_{\text{GS}} + C_{\text{osci}} = \frac{V_S}{k_{0+} R_L} = 175.2225 \mu\text{F} \quad (14.18)$$

If oscilloscope input capacitance  $C_{\text{osci}}$  is about 15 pF, then we have  $C_{\text{GS}} \approx 160 \mu\text{F}$ .

**The Delay Used as a Digital Inverter**

Let  $C_{GS} \approx 160 \mu\text{pF}$ ,  $V_T = 1.85 \text{ V}$ ,  $V_0 + \Delta V = 3.22 \text{ V}$   $V_I = 5 \text{ V}$ , yielding:

$$\begin{cases} \Delta t = \tau \ln \left( \frac{V_S}{V_S} - V_T \right) \\ \tau = \frac{R_1 R_2}{R_1 + R_2} C \\ V_S = \frac{R_2}{R_1 + R_2} \cdot V_I \end{cases} \implies \text{start to fall: } \Delta t_1 = 0.1287 \mu\text{s}, \quad \text{reach low: } \Delta t_2 = 1.3040 \mu\text{s} \quad (14.19)$$