

电子电路手册

Electronic Circuits Manual

丁毅

(中国科学院大学, 北京 100049)

Yi Ding

(University of Chinese Academy of Sciences, Beijing 100049, China)

2024.11 – ...

序言

Preface

Contents

序言	I
Preface	II
Contents	III
1 Capacitance	1
1.1 Large Capacitor	1
1.1.1 Capacitance Multiplier	1
1.2 Small Capacitor	1
1.3 Variable Capacitor	2
2 Inductance	3
Reference	4

Chapter 1 Capacitance

1.1 Large Capacitor

1.1.1 Capacitance Multiplier

This part refers to references [1] and [2]. Below are two basic concepts for capacitance multiplication:

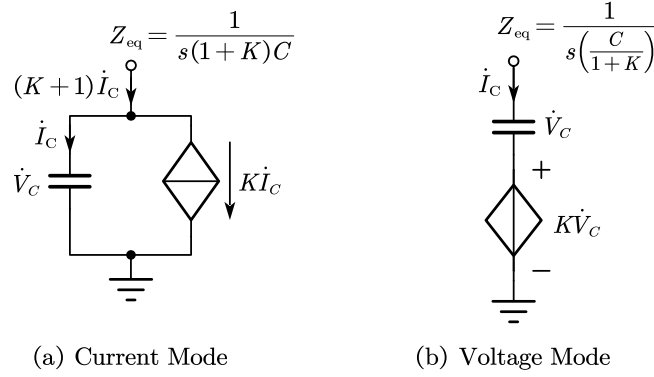


Figure 1.1: Basic Capacitance Multiplier Circuits

Thus, we obtain the equivalent capacitance as:

$$\text{Current Mode: } C_{eq} = (1 + K)C \Rightarrow \begin{cases} C_{eq} > C, & K > 0 \\ C_{eq} < C, & K < 0 \end{cases} \quad (1.1)$$

$$\text{Voltage Mode: } C_{eq} = \frac{C}{1 + K} \Rightarrow \begin{cases} C_{eq} < C, & K > 0 \\ C_{eq} > C, & K < 0 \end{cases} \quad (1.2)$$

A simple implementation of cap multiplier, depicted in Fig.1.2, combining a unit-gain buffer (voltage follower) and an inverting amplifier, is a voltage mode circuit. yielding the equivalent capacitance:

$$C_{eq} = \frac{C}{1 + K} = \frac{1}{1 - \frac{R_2}{R_1}} = \frac{R_1}{R_1 - R_2} C \quad (1.3)$$

where $K = -\frac{R_2}{R_1}$ is the closed-loop gain of the inverting amplifier. Since inverting amplifier has a low input impedance, the unit-gain buffer is a necessary. To change it into a two-terminal element, just replace GND with the negative terminal of the input voltage, e.g. $V_{in,-}$.

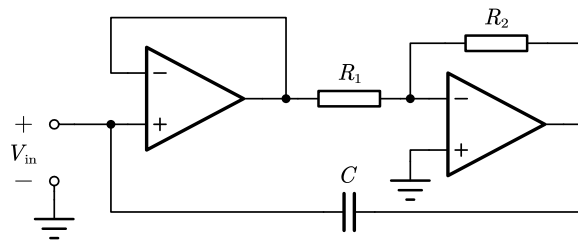


Figure 1.2: A Simple Implementation of Capacitance Multiplier

1.2 Small Capacitor

1.3 Variable Capacitor

Chapter 2 Inductance

Reference

- [1] Gabriel Bonteanu. A Review of Capacitance Multiplication Techniques. In *2018 10th International Conference on Electronics, Computers and Artificial Intelligence (ECAI)*, pages 1–4, 2018. <https://ieeexplore.ieee.org/document/8678969>.
- [2] Ivan Padilla-Cantoya, Luis Rizo-Dominguez, and Jesus E. Molinar-Solis. Capacitance multiplier with large multiplication factor, high accuracy, and low power and silicon area for floating applications. *IEICE Electronics Express*, 15(3):20171191–20171191, 2018. <https://doi.org/10.1587/elex.15.20171191>.
- [3] Behzad Razavi. *Fundamentals of Microelectronics*. University of California Press, 2nd edition, 2014.
- [4] Behzad Razavi. *Design of Analog CMOS Integrated Circuits*. McGraw-Hill Education, 2nd edition, 2017.